 


Problem 1(40pts):

Figure P1 shows the logic diagram and the corresponding description for a synchronous sequential circuit.



(a) Diagram

```

module main(G0,G1,G2,G3,G17);
input G0;
input G1;
input G2;
input G3;

output G17;
wire G5,G6,G7,G14,G8,G12,
      G15,G16,G13,G9,G11,G10;

dff1 XG1 (G5,G10);
dff1 XG2 (G6,G11);
dff1 XG3 (G7,G13);
not XG4 (G14,G0);
and XG5 (G8,G6,G14);
nor XG6 (G12,G7,G1);
or XG7 (G15,G8,G12);
or XG8 (G16,G8,G3);
nor XG9 (G13,G12,G2);
nand XG10 (G9,G15,G16);
nor XG11 (G11,G9,G5);
nor XG12 (G10,G11,G14);
not XG13 (G17,G11);

end
endmodule

```

(b) Circuit description

Figure P1: ISCAS s27 benchmark circuit

The ISCAS benchmark circuit description, shown in **Figure P1(b)**, consists of set of lines. Every line describes how one logic gate is interconnected with other gates. For example, line 'G5 = DFF(G10)' indicates the existence of a D-type Flip-flop with output G5 (connected to the state line q) and input G10 (connected to d). In this description INPUT (G1)/OUTPUT (G17); indicates that line G1 is a primary input/line G17 is a primary output.

Gate name	Gate type	List of pointers to fanin	List of pointer to fanout	Pointer to the next gate
-----------	-----------	---------------------------	---------------------------	--------------------------

Figure P2: Data record

- Write a (C or C++) computer program that reads in the ISCAS circuit description, adds buffers as needed and stores it in the data structure shown in **Figure P2**. To add buffers, for every fanout branch add a buffer gate and modify your data structure to reflect the change. **Figure P3** shows an AND gate with two fanout branches and the AND gate after adding the two buffers. (Add also buffers if needed for output nodes)
- For every gate in the modified circuit associate a 'level'. The gate 'level' indicates the distance of that gate from primary inputs or pseudo inputs (D flip-flop Q's). Initially, the level of primary inputs and DFF flip-flops are set to zero. Gates 'level' for other gates are set to a negative value indicating uninitialized 'level'. Then, the a gate 'level', with assigned positive value on all of its inputs, is equal to the maximum 'level' of its inputs plus one. This step

**Figure P3: Fanout branches**

is repeated until every gate 'level' is assigned a positive number.

- c) Your program should prints the following: The total number of gates stored including buffers, the number of gates assigned level n, and a listing of the final stored in the intermediate format shown below.

GateType	Output	GateLevel	#faninN	fin1	fin2	...	finN	#fanoutM	fout1	fout2	...	foutM	GateName
----------	--------	-----------	---------	------	------	-----	------	----------	-------	-------	-----	-------	----------

Problem 2 (60pts): The intermediate file consists of lines where each line represents a gate in the circuit.

In this format, each gate has a name except the added buffers.

- (b) Use 3-valued logic { 0, 1, X } to create a two inputs lookup tables for the following gates AND, OR, XOR, and NOT. Gates with more than two inputs can be evaluated by repeated evaluation using the two inputs table lookup.
- (c) Add to every gate structure a pointer 'sched' and set that pointer initially to zero. This pointer should be used to schedule the corresponding gate. Create a dummy gate structure and keep a pointer to it in variable 'dummy_gate'.
- (d) Create an array 'levels' of pointers to a gate structure of size 'max level'. 'max_level' is an integer holding the value of max level in your design. Initially, levels[i] is set to dummy gate for all i's.
- (e) Use 3-valued logic {0, 1, X} to create two inputs lookup tables for the following gates AND, OR, XOR, and NOT. Gates with more than two inputs can be evaluated by more than one table lookup.
- (f) To schedule events due to a change of the state of gate i:
- For each gate f in the fanout list of gate i, if the field 'sched' of gate f is zero, then insert f at the head of the list at the corresponding level. Otherwise, no action is needed (schedule_fanout(gaten) in **Figure P4**).
- (g) Implement the algorithm shown in **Figure P5**. In this algorithm, Flip-Flop do not need to be scheduled:

```

schedule_fanout(g)
{
    N = gate[g].nfanout;
    for( i=0 ; I < N ;i++ ){
        fg = gate[g].fanout[i];
        if ( gate[fg].next !=
dummy_gate){
            fg_level = gate[fg].level;
            gate[fg].next = level[fg_level];
            level[fg_level]=fg;
        }
    }
}

```

Figure P4: Schedule fanout

```

while() {
    print logic values at PI, PO, and States
    read inputs and schedule fanouts of changed
    inputs.
    load next state and schedule fanout.
    i = 0;
    while( i < max level) {
        gaten = levels[i];
        while( gaten != dummy_gate ) {
            newstate = evaluate( gate);
            if( new_state != gate.state ) {
                gate[gaten].state = new_state ;
                schedule_fanout( gaten );
            }
            tempn = gaten ;
            gaten = gate[gaten].sched ;
            gate[gaten].sched = 0 ;
            gaten = tempn;
        }
        levels[i] = gaten ;
        i = i + 1 ;
    }
}

```

Figure P5: Simulation Flow

Implement the 'evaluate' routine using the two techniques discussed in class:

d) Input scanning:

Controlling value 'c'
and inversion 'i'

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

```

evaluate(Gn){
    Uvalue = FALSE
    for(i=0; i<gate[Gn].nfanin;i=i+1){
        V = gate [ gate[Gn].fanin[i] ].state;
        if( V = c ) return( c ⊗ i)
        if( V = X) Uvalue = TRUE;
    }
    if( Uvalue ) return X; else return  $\bar{c} \otimes i$ ;
}

```

e) Table lookup:

```

evaluate(Gn){
    state_fanin0 = gate[ gate[Gn].fanin[0] ].state ;
    gate_type = gate[Gn].gtype;

```

```

if gate_type == INV then return Inv_table[ state_fanin0 ];
if gate_type == BUF then return state_fanin0 ;
state_fanin1 = gate[ gate[Gn].fanin[1] ].state ;
v = Table[gate_type][ state_fanin0 ][ state_fanin1 ]
nfanin = gate[Gn].nfanin;
for( i = 2; i < nfanin ; i++) {
    state_fanin0 = gate[ gate[Gn].fanin[i] ].state ;
    v = Table[gate[Gn].gate_type][ state_fanin0 ][ v ] ;
}
If( gate[Gn].i ) return (Inv_table[v]; else return ( v ) ;
}

```

- f) Record the CPU time your program requires to run both examples circuit posted on the website using the input scanning and table-lookup. Compare the two techniques.

Here is an input/output for s27

input file for s27: G0, G1, G2, G3

```

0000
0010
0100
1000
1111

```

```

INPUT   :0100
STATE   :040
OUTPUT  :4

```

output file: 4 represents undefined

```

INPUT   :0000 // G0, G1, G2, G3
STATE   :444  // G5, G6, G7
OUTPUT  :4    // G17

```

```

INPUT   :1000
STATE   :041
OUTPUT  :1

```

```

INPUT   :0010
STATE   :044
OUTPUT  :4

```

```

INPUT   :1111
STATE   :101
OUTPUT  :1

```